

ICS53 - MIPS Instruction Set Architecture & Single-Cycle Datapath (continued)

Branch on Equal

Ex: beq \$t0, \$s0, label # if Reg[\$t0] == Reg[\$s0], then PC = PC + 4 + label



Branch on Equal Instruction Walk-through

I-type

| op | rs | rt | imm |
|--------|--------|--------|---------|
| 6 bits | 5 bits | 5 bits | 16 bits |

- These instructions take two operands from registers and perform an ALU comparison operation on them, if the operation is “true” then the PC is replaced with the location of the next instruction to execute.
- The label value in the immediate field from the instruction, is not the 32-bit address of the label. Instead the field represents +/- the number of instructions from the PC+4 address.
 - Most branch statements are local jumps for loops and conditional checks. These jumps are not too far of places in memory. Therefore, +/- 2^{15} instructions is more than enough range.
 - Note, how it is the number of instructions, not the number of bytes. Since all label addresses are multiples of 4, we can increase the range by eliminating the need to store the LSB 00 in the immediate field. Instead we shift the immediate field to the left by 2 to multiple the value by 4.
 - Note, the calculation of the relative position of the branch label is performed based on the PC+4 value, not the current instruction. The reason for this will become clear in the next module. For now, just accept this fact.

Assignment Project Exam Help

Branch

<https://powcoder.com>


Fetch – Register Read (rs: \$s0, rt: \$t0),
Sign Extend Immediate Value

Execute – Compare operands by performing
subtract ALU operation (Reg[\$s0] – Reg[\$t0])

Execute – If “true” (Zero == 1), set PC value to
target address

- In the execute stage, we subtract the register values and check to see if the result is 0 using the Zero output of the ALU. Remember, the Zero output has a value of 1 if the result of the ALU is 0, 0 otherwise.
- While the operands are being compared, the target address (the location of the next instruction to execute if branch is “true”) is calculated by:
 - Sign-extend the immediate value (positive or negative 2’s complement value)
 - Shift left 2 places (multiply by 4 to get word address)
 - Add value to PC + 4 value
- Note that for the branch operation, we use the PCBranch adder to calculate the branch address.
 - This is because the entire datapath must execute in a single clock cycle. This means that each component of the datapath can only perform 1 operation. **Hardware cannot be reused in the same instruction during the clock cycle.**

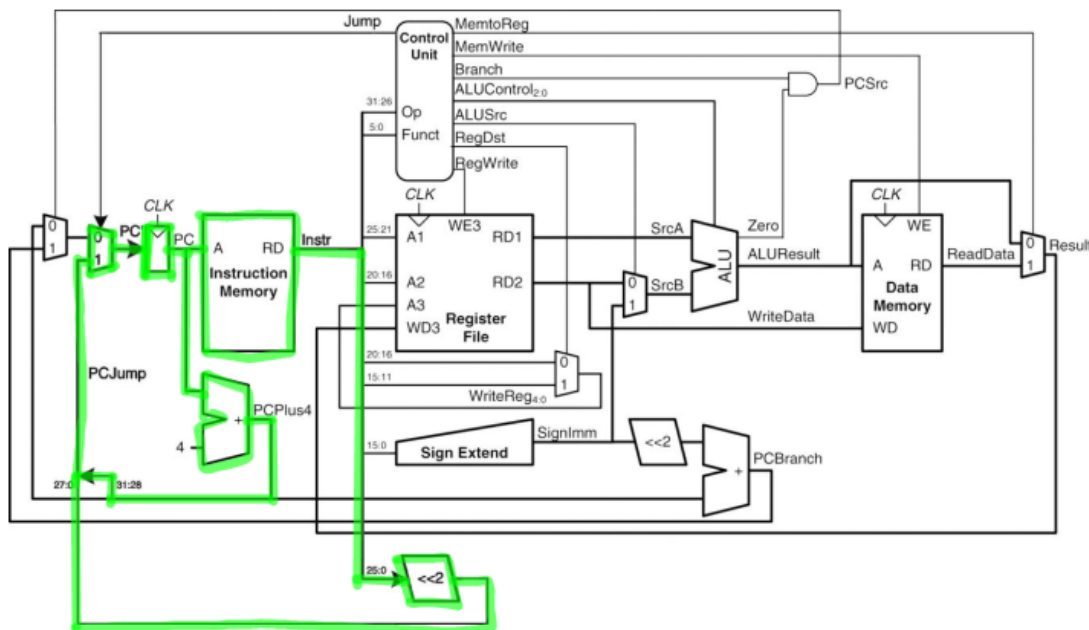- 26-bit address field in instruction
- 00 as the 2 low-order bits (word address, not byte. Therefore, multiply by 4.)



Control Unit

Assignment Project Exam Help




[Single-Cycle Control Unit](https://powcoder.com)

<https://powcoder.com>

- The names of the control signals are named to represent flags, eg. Branch = 1 means branch is true/taken, Branch = 0 means branch is false/not taken.
 - A signal is asserted = 1 or deasserted = 0
- The complete Control Table the 5 basic operations implemented in the datapath is shown below:


Add WeChat powcoder

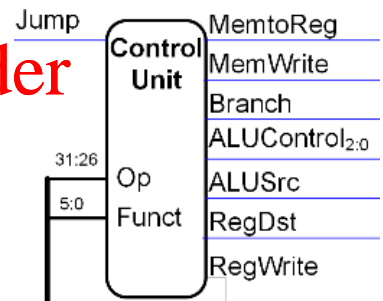

| Instr | Opcode | RegDst | RegWrite | ALUSrc | MemRead | MemWrite | MemtoReg | Branch | ALUOp | Jump |
|--------|--------|--------|----------|--------|---------|----------|----------|--------|-----------|------|
| lw | 100011 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 00 (add) | 0 |
| sw | 101011 | X | 0 | 1 | 0 | 1 | X | 0 | 00 (add) | 0 |
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 10 (func) | 0 |
| beq | 000100 | X | 0 | 0 | 0 | 0 | X | 1 | 01 (sub) | 0 |
| jump | 000010 | X | 0 | X | 0 | 0 | X | X | XX | 1 |

- Note the ALUOp column of the table. This value is a 2-bit control determined within the Control Unit and is used to create the 3-bit ALUControl output for the ALU.
- Because the ALU control is based on not only the opcode, but the function field (R-type), the control logic unit is split into 2 steps.
 - This reduces the number of inputs for the ALUOperation Boolean expression from 12-bits (6 for opcode and 6 for func field) to 8-bits (2 for intermediate ALUOp and 6 for func field)

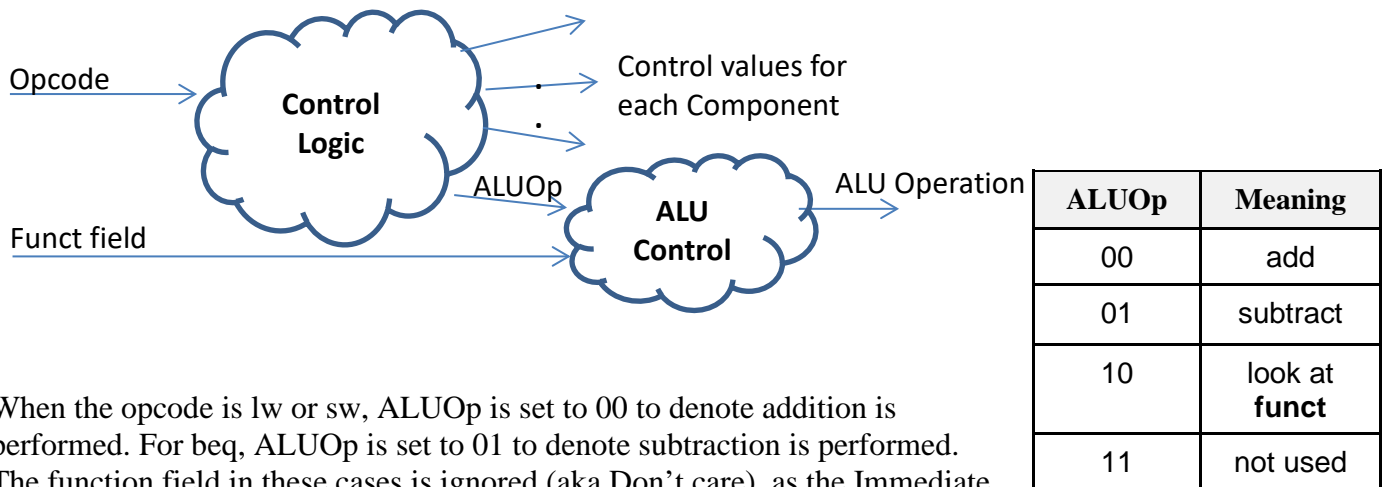- Based on the opcode a 2-bit control value, ALUOp, can be created as an intermediate output. This value then combined with the function field produces the proper ALU Operation control.



- When the opcode is lw or sw, ALUOp is set to 00 to denote addition is performed. For beq, ALUOp is set to 01 to denote subtraction is performed. The function field in these cases is ignored (aka Don't care), as the Immediate instruction format do not contain a function field.
- In the case of R-type instructions, the function field is the unique identifier for the operation (remember that the opcode is set to all zeros in the case of R-type instructions).
 - The ALUOp is set to 10, to denote the function field should be considered when determining the ALUControl.

| opcode | ALUOp | Operation | funct | ALU function | ALU control |
|--------|-------|------------------|--------|------------------|-------------|
| lw | 00 | load word | XXXXXX | add | 010 |
| sw | 00 | store word | XXXXXX | add | 010 |
| beq | 01 | branch equal | XXXXXX | subtract | 110 |
| R-type | 10 | add | 100000 | add | 010 |
| | | subtract | 100010 | subtract | 110 |
| | | AND | 100100 | AND | 000 |
| | | OR | 100101 | OR | 001 |
| | | set-on-less-than | 101010 | set-on-less-than | 111 |

- !!** In all of the discussions/practice problems/notes we use the 2-bit ALUOp to denote the operation performed by the ALU unit instead of the 3-bit ALUControl (less to remember).